
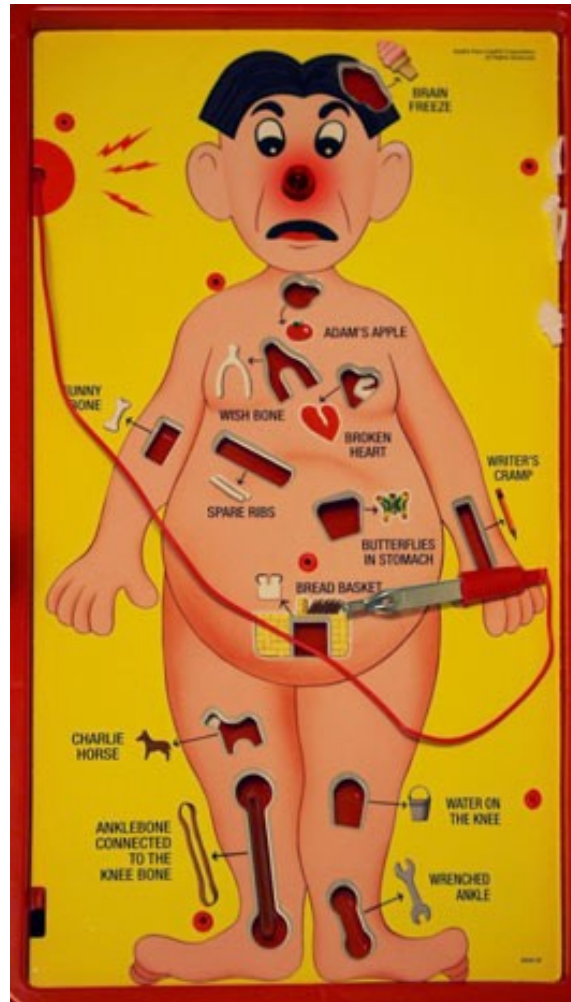


How does the circuit work in Operation?

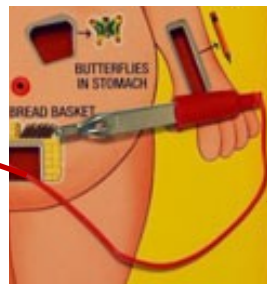


Electrons flow from battery through the wire on the tweezers.



If the metal tweezers touch the metal area around the opening, this closes the circuit.



Current returns to the battery.

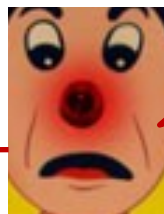

Electrical current flows through, sounding the buzzer and lighting the light